



National  
Qualifications  
2024

---

**2024 Engineering Science**

**Higher**

**Question Paper Finalised Marking Instructions**

© Scottish Qualifications Authority 2024

These marking instructions have been prepared by examination teams for use by SQA appointed markers when marking external course assessments.

The information in this document may be reproduced in support of SQA qualifications only on a non-commercial basis. If it is reproduced, SQA must be clearly acknowledged as the source. If it is to be reproduced for any other purpose, written permission must be obtained from [permissions@sqa.org.uk](mailto:permissions@sqa.org.uk).




## General marking principles for Higher Engineering Science


Always apply these general principles. Use them in conjunction with the detailed marking instructions, which identify the key features required in candidates' responses.


- (a) Always use positive marking. This means candidates accumulate marks for the demonstration of relevant skills, knowledge and understanding; marks are not deducted for errors or omissions.
- (b) If a specific candidate response does not seem to be covered by either the principles or detailed marking instructions, and you are uncertain how to assess it, you must seek guidance from your team leader.
- (c) Where a candidate makes an error at an early stage in a multi-stage calculation, award marks for correct follow-on working in subsequent stages. Do not award marks if the error significantly reduces the complexity of the remaining stages. Apply the same principle in questions which require several stages of non-mathematical reasoning.
- (d) SQA presents all units of measurement in a consistent way, using negative indices where required (for example  $\text{ms}^{-1}$ ). Candidates can respond using this format, or solidus format (m/s), or words (metres per second), or any combination of these (for example metres/second).
- (e) For numerical questions, candidates should round their answers to an appropriate number of significant figures. However, award marks if their answer has up to two figures more or one figure less than the expected answer.
- (f) Unless a numerical question specifically requires candidates to show evidence of their working, award full marks for a correct final answer (including unit) on its own.
- (g) Award marks where a labelled diagram or sketch conveys clearly and correctly the response required by the question.
- (h) Award marks regardless of spelling if the meaning is unambiguous.
- (i) Candidates can answer programming questions in any appropriate programming language. Award marks where the intention of the coding is clear, even where there are minor syntax errors.
- (j) For 'Explain' questions, only award marks where the candidate goes beyond a description, for example by giving a reason, or relating cause to effect, or providing a relationship between two aspects.
- (k) Where separate space is provided for rough working and a final answer, only award marks for the final answer. Ignore all rough working.


## Marking instructions for each question

### Section 1
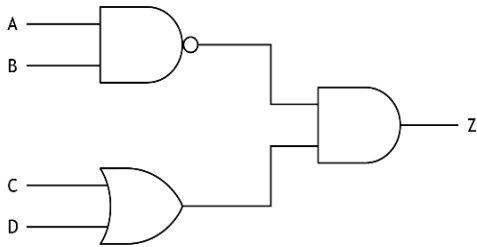
| Question |  |  | Expected response                                                                                                                                                                                                                                                                                                                          | Max mark | Additional guidance                                                                                                                                                                                        |
|----------|--|--|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 1.       |  |  |                                                                                                                                                                                                                                                           | 3        | <p>1 mark for NAND (AND and NOT) with connections.</p> <p>1 mark for OR with connections.</p> <p>1 mark for AND with connections.</p> <p>NAND equivalents also accepted.</p>                               |
| 2.       |  |  | $T = Fr$<br>$T = ((76+95+18) \times 9.8) \times (0.84 / 2)$<br>$T = 777.924 \text{ Nm}$<br><b><math>T = 780 \text{ Nm (2 sf)}</math></b>                                                                                                                                                                                                   | 2        | <p>1 mark for correct substitution.</p> <p>1 mark for correct answer (FTE).</p>                                                                                                                            |
| 3.       |  |  | <p>UDL point load = <math>1.8 \times 8.3 = 14.94 \text{ kN @ } 4.15\text{m}</math></p> <p>Take moments about A:<br/> <math>(3.8 \sin 62 \times 5.8) + (14.94 \times 4.15) = 8.3 R_B</math><br/> <math>81.46116495 = 8.3 R_B</math><br/> <math>R_B = 9.814598187 \text{ kN}</math><br/> <b><math>R_B = 9.8 \text{ kN (2 sf)}</math></b></p> | 4        | <p>1 mark for UDL value 14.94 (unit not required).</p> <p>1 mark for <math>3.8\sin 62</math> (or <math>3.8\cos 28</math>).</p> <p>1 mark for correct substitution.</p> <p>1 mark for <math>R_B</math>.</p> |
| 4.       |  |  | $V_o = -18 (5/54 + 5/36 + 5/18)$<br>$V_o = -9.166666667 \text{ V}$<br><b><math>V_o = -9.2 \text{ V (2 sf)}</math></b>                                                                                                                                                                                                                      | 2        | <p>1 mark for correct substitution.</p> <p>1 mark for correct answer.</p>                                                                                                                                  |
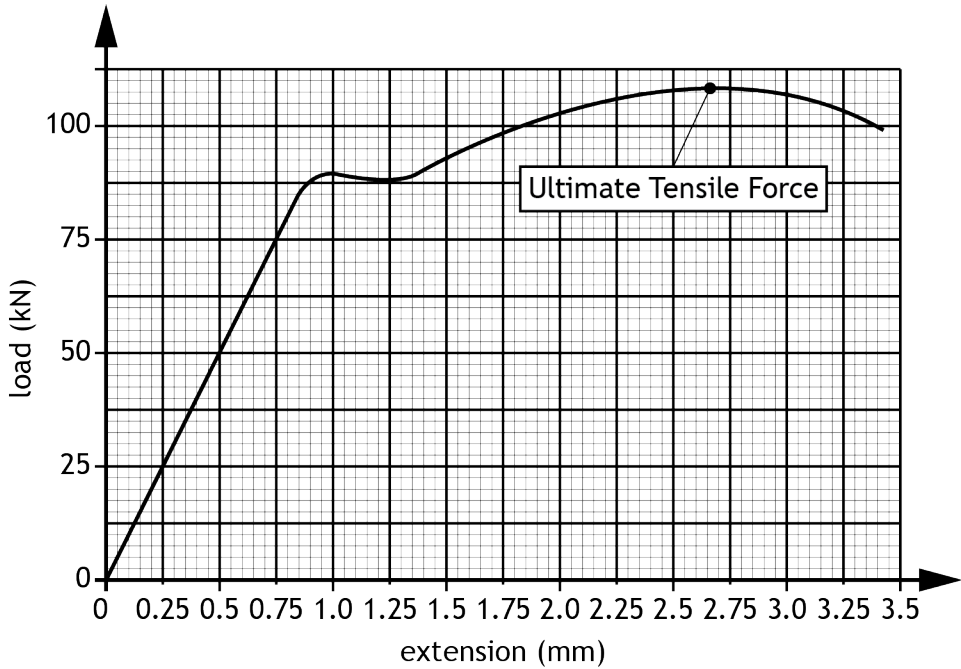
| Question |     |                                                                                                                                       | Expected response                                                                  | Max mark | Additional guidance                                                |
|----------|-----|---------------------------------------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------|----------|--------------------------------------------------------------------|
| 5.       | (a) |                                                                                                                                       |  |          |                                                                    |
|          |     |                                                                                                                                       |                                                                                    | 1        | 1 mark for correct annotation on graph.                            |
|          | (b) | $E_s = \frac{1}{2} Fx$<br>$E_s = 0.5 \times 75 \times 10^3 \times 0.00075$<br>$E_s = 28.125 \text{ J}$<br>$E_s = 28 \text{ J (2 sf)}$ |                                                                                    | 2        | 1 mark for correct substitution.<br><br>1 mark for correct answer. |
|          | (c) | The material stretches and then returns to its original length.                                                                       |                                                                                    | 1        |                                                                    |
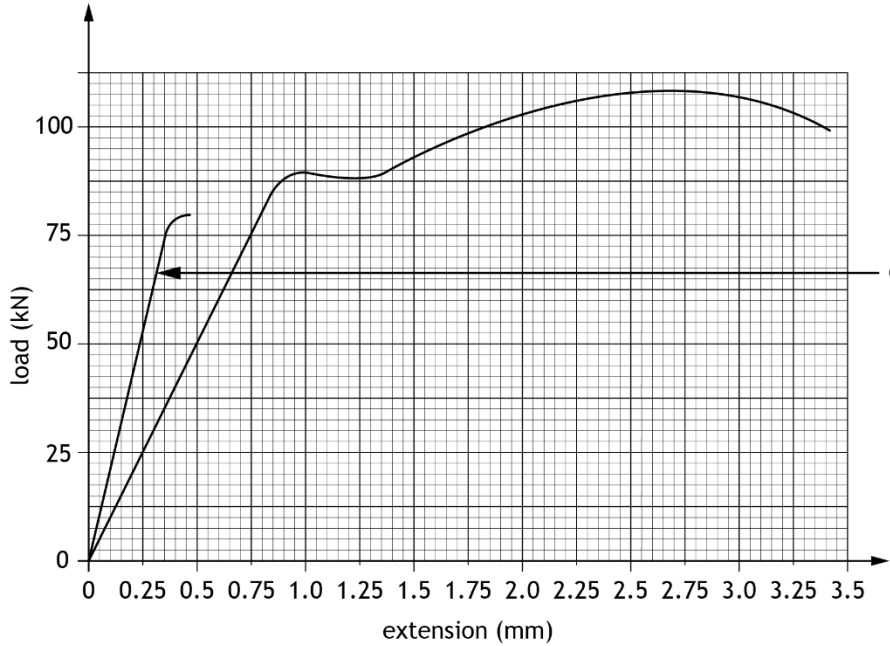
| Question |     |  | Expected response                                                                                                                            | Max mark | Additional guidance                                                                                                                                                                                                                |
|----------|-----|--|----------------------------------------------------------------------------------------------------------------------------------------------|----------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 5.       | (d) |  | A graph that shows very little extension beyond yield point.                                                                                 | 1        | Further guidance on acceptable responses:<br>Graph may be similar to classic trace for cast iron.<br>Graph may have straight line gradient (gradient and E value not important) with no or little plastic region prior to failure. |
|          |     |  | <p>eg:</p>  <p>example of expected candidate response</p> |          |                                                                                                                                                                                                                                    |
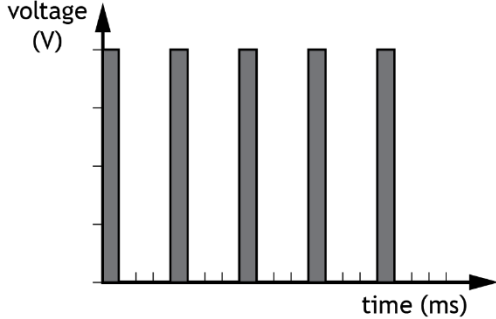
| Question |     |  | Expected response                                                                                                                                                                     | Max mark | Additional guidance                                                                                                                                                                                                                                                                                           |
|----------|-----|--|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 6.       | (a) |  | <p>Correction 1<br/> PBBASIC: if pin 1 = 0 then main<br/> ARDUINO: if digitalWrite(pin1)==LOW){<br/> loop();}</p> <p>Correction 2<br/> PBBASIC: pause 45<br/> ARDUINO: delay(45);</p> | 2        | <p>1 mark for Correction 1.<br/> Also accept: if pin 1 = 1 then pwm<br/> (must be followed by 'goto main')</p> <p>OR: if digitalWrite(pin1)==HIGH){<br/> pwm();}<br/> (must be followed by 'return')</p> <p>1 mark for Correction 2.</p> <p>The same correction may not be given for two different codes.</p> |
|          | (b) |  |                                                                                                     | 2        | <p>1 mark for marks with same voltage.</p> <p>1 mark for all three correct mark:space ratio.</p> <p>Response must include minimum of three marks and two spaces to establish correct duty cycle.</p>                                                                                                          |


## Section 2

| Question |     |      | Expected response                                                                                                                                                                                                                                                                                                                                                                                                                                                                                             | Max mark | Additional guidance                                                     |
|----------|-----|------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|-------------------------------------------------------------------------|
| 7.       | (a) |      | <p>Fault:<br/>Pilot actuator on <math>V_1</math>.</p> <p>Correction:<br/>Replace with diaphragm actuator.</p> <p>Fault:<br/>No delay between <math>C_A</math> outstroking and <math>C_B</math> &amp; <math>C_C</math> outstroking (<math>V_1</math> and <math>V_2</math>).</p> <p>Correction:<br/>Connect UDR and reservoir in series between <math>V_1</math> and <math>V_2</math>.</p> <p>Fault:<br/>Time delay not connected correctly.</p> <p>Correction:<br/>UDR and reservoir to be swapped around.</p> | 6        | 1 mark for identifying each fault.<br>1 mark for each correct solution. |
|          | (b) | (i)  | <p>Components are hard wearing/more reliable, so fewer waste products.</p> <p>Components are hard wearing/more reliable, so fewer materials need to be mined for manufacture.</p> <p>The exhaust air causes no pollution.</p> <p>System is more energy efficient when supplied from stored air.</p> <p>Less oil is used, so there is a reduction in environmentally harmful waste products.</p>                                                                                                               | 2        |                                                                         |
|          |     | (ii) | <p>Using equations to calculate the forces/pressures/areas of cylinders.</p> <p>Using equations to calculate mechanical power.</p> <p>Using equations to calculate reservoir volume/time delay.</p>                                                                                                                                                                                                                                                                                                           | 1        |                                                                         |

| Question |     |  | Expected response                                                                                                                                                                                                                                                                                                                                                                                                                                                                                   | Max mark | Additional guidance                                                                                                                                                                                                                                                                           |
|----------|-----|--|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 7.       | (c) |  | $I_{DS} = (6-5.2)/2.9$<br>$= 0.275862069 \text{ A}$<br><br>$V_{GS} = 4.2 \text{ V (2 sf)}$                                                                                                                                                                                                                                                                                                                                                                                                          | 3        | 1 mark for calculating voltage across solenoid.<br><br>1 mark for calculating $I_{DS}$ .<br><br>1 mark for identifying $V_{GS}$ .                                                                                                                                                             |
|          | (d) |  | <pre> graph TD     Start([start]) --&gt; Pin1{pin 1 on?}     Pin1 -- N --&gt; Start     Pin1 -- Y --&gt; Pin6On[/pin 6 on/]     Pin6On --&gt; Reading{is reading &lt;50 or &gt;100?}     Reading -- N --&gt; Pin7On[/pin 7 on/]     Pin7On --&gt; Pause[pause 1s]     Pause --&gt; Pin7Off[/pin 7 off/]     Pin7Off --&gt; Sheets{10 sheets?}     Sheets -- N --&gt; Pin1     Sheets -- Y --&gt; Pin6Off[/pin 6 off/]     Pin6Off --&gt; Stop([stop])     Reading -- Y --&gt; Pin1           </pre> | 5        | Choosing correct conditions for pneumatic action - 1 mark.<br><br>Loop to start after checking analogue sensor - 1 mark.<br><br>Pneumatic control (pin 7 on/pause 1s/pin 7 off) - 1 mark.<br><br>'10 sheets?' decision with correct loop and stop - 1 mark.<br><br>Pin 6 off and on - 1 mark. |




| Question |     |  | Expected response                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                  | Max mark | Additional guidance                                                                                                                                                               |
|----------|-----|--|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 8.       | (a) |  | $R_A/R_B = R_1/R_2$<br>$119/120 = R_1/1000$<br>$R_1 = (119 \times 1000)/120$<br>$= 991.6666667 \Omega$<br>$= 990 \Omega$ (2 sf)                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                    | 2        | 1 mark for recognising the relationship between the two input voltages.<br><br>1 mark for correct answer with unit.                                                               |
|          | (b) |  | It counteracts the impact of expansion/contraction due to temperature changes in the system.<br><br>Passive strain gauge B serves to enhance the accuracy and reliability of strain measurements.<br><br>Strain gauge B acts as a reference for the active strain gauge.                                                                                                                                                                                                                                                                                                                                                           | 1        |                                                                                                                                                                                   |
|          | (c) |  | $5 \times 0.85 = 4.25 \text{ V}$<br>$I_b = (4.25 - 0.7) / 1200$<br>$= 0.00295833 \text{ A}$<br>$I_c = 0.00295833 \times 320$<br>$= 0.94666667 \text{ A}$<br>$= 0.95 \text{ A}$ (2 sf)                                                                                                                                                                                                                                                                                                                                                                                                                                              | 4        | 1 mark for output from op-amp.<br><br>1 mark for voltage across resistor.<br>1 mark for $I_b$ .<br><br>1 mark for $I_c$ .                                                         |
|          | (d) |  | <b>Range = 1.1 V to 3.9 V</b><br><br>Motor will turn when both op-amps are on. $V_{in}$ must be greater than $V_{refB}$ and less than $V_{refA}$ .<br><br>$V_{refB} = 5 \times 1.2 / (1.2 + 3.3 + 1.2)$<br>$= 1.052631579 \text{ V}$<br>$= 1.1 \text{ V}$ (2 sf)<br><br>$V_{refA} = 5 \times 4.5 / (1.2 + 3.3 + 1.2)$<br>$= 3.947368421 \text{ V}$<br>$= 3.9 \text{ V}$ (2 sf)<br><br>Alternative method:<br><br>$V_{CC} / R_1 = V_{refA} / R_A$<br>$5 / 5700 = V_{refA} / 4500$<br>$V_{refA} = 3.95 \text{ V}$ (2 sf)<br><br>$V_{CC} / R_t = V_{refB} / R_B$<br>$5 / 5700 = V_{refB} / 1200$<br>$V_{refB} = 1.1 \text{ V}$ (2 sf) | 3        | 1 mark for identifying the range (units not required, FTE applies).<br><br><br><br><br><br>1 mark for calculating $V_{refB}$ .<br><br><br><br>1 mark for calculating $V_{refA}$ . |
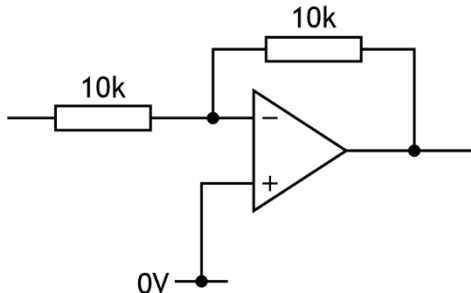
| Question |     |      | Expected response                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                               | Max mark | Additional guidance                                                                                                                                                                                                                                                                              |
|----------|-----|------|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 8.       | (e) |      | <p>When <math>V_{in}</math> is 0V, op-amp B is off and op-amp A is on, therefore MOSFET B is switched off and MOSFET A is switched on, so the motor is off.</p> <p>When <math>V_{in}</math> is more than <math>V_{refB}</math> but less than <math>V_{refA}</math>, both op-amps are on, so both MOSFETs are switched on and the motor is on.</p> <p>When <math>V_{in}</math> is greater than <math>V_{refA}</math>, op-amp B is on and op-amp A is off, therefore MOSFET B is on and MOSFET A is off, so the motor is off.</p> | 3        | <p>1 mark for: description of op-amp B off, MOSFET B off, motor off, under the correct conditions.</p> <p>1 mark for: description of all components on, under the correct conditions.</p> <p>1 mark for: description of op-amp A off, MOSFET A off, motor off, under the correct conditions.</p> |
|          | (f) | (i)  | $-2.7 = -R_f \times ((0.012/33000) + (0.017/33000) + (0.026/33000) + (0.024/33000))$ $R_f = 1127848.101 \, \Omega$ $= 1.1 \, M\Omega \, (2 \, sf)$                                                                                                                                                                                                                                                                                                                                                                              | 2        | <p>1 mark for correct substitution.</p> <p>1 mark for correct answer from given working.</p>                                                                                                                                                                                                     |
|          |     | (ii) |                                                                                                                                                                                                                                                                                                                                                                                                                                              | 2        | <p>1 mark for inverting op-amp with all connections.</p> <p>1 mark for <math>R_f</math> and <math>R_i</math> being the same value. Units required.</p>                                                                                                                                           |


| Question |     |  | Expected response                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                          | Max mark | Additional guidance                                                                                                                                                                      |
|----------|-----|--|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 9.       | (a) |  | $T = Fr$<br>$T = 240 \times 0.30$<br>$T = 72 \text{ Nm}$<br><br>$P = VI$<br>$P = 220 \times 6.6$<br>$P = 1452 \text{ W}$<br><br>$P = 2 \times \pi \times n \times T$<br>$1452 = 2 \times \pi \times n \times 72$<br>$n = 1452 / (2 \times \pi \times 72)$<br>$n = 3.209624686 \text{ revs sec}^{-1}$<br>$n = 3.2 \text{ revs sec}^{-1} \text{ (2 sf)}$                                                                                                                                                                                                                                                                                                     | 4        | <p>1 mark for calculating torque.</p> <p>1 mark for calculating power.</p> <p>1 mark for substitution.</p> <p>1 mark for calculating n, unit required.</p>                               |
|          | (b) |  | <p>Total working stress on bolt<br/> <math>= (\text{UTS}/\text{FOS})</math><br/> <math>= (430/3.0)</math><br/> <math>= 143.3333333 \text{ Nmm}^{-2}</math></p> <p>Safe working stress on bolt<br/> <math>= 143.3333333 - 5.5</math><br/> <math>= 137.8333333 \text{ Nmm}^{-2}</math></p> <p>Cross-sectional area of bolt<br/> <math>A = F/\sigma</math><br/> <math>= 5000/137.8333333</math><br/> <math>= 36.27569529 \text{ mm}^2</math></p> <p>Diameter of bolt<br/> <math>d = \sqrt{4A/\pi}</math><br/> <math>d = \sqrt{(4 \times 36.27569529)/\pi}</math><br/> <math>d = 6.796149628 \text{ mm}</math><br/> <math>d = 6.8 \text{ mm (2.sf)}</math></p> | 4        | <p>1 mark for SWS.</p> <p>1 mark for subtracting 5.5.</p> <p>1 mark for area, apply FTE if 143.3333333 used.</p> <p>1 mark for required diameter, unit required.</p>                     |
|          | (c) |  | <p>2500 litres = 2500 kg</p> <p><math>E_w = Fd</math><br/> <math>E_w = (2500 \times 9.8) \times 2.9</math><br/> <math>E_w = 71050 \text{ J}</math></p> <p><math>E_{ff} = E_{out} / E_{in}</math><br/> <math>E_{in} = 71050 / 0.87</math><br/> <math>E_{in} = 81666.66667 \text{ J}</math></p> <p><math>E_e = VIt</math><br/> <math>81666.66667 = 230 \times 5 \times t</math><br/> <math>t = 71.01449275 \text{ s}</math><br/> <math>t = 71 \text{ s (2 sf)}</math></p>                                                                                                                                                                                    | 4        | <p>1 mark for <math>E_w</math> (<math>E_{out}</math>).</p> <p>1 mark for <math>E_{in}</math> (<math>E_e</math>).</p> <p>1 mark for substitution.</p> <p>1 mark for t, unit required.</p> |

| Question |     |  | Expected response                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                               | Max mark | Additional guidance                                                                                                                                                                            |
|----------|-----|--|---------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 9.       | (d) |  | $A = F / \sigma$<br>$A = 625 / 3.4$<br>$A_{\text{effective}} = 183.8235294 \text{ mm}^2$<br><br>$A_{\text{effective}} = A_{\text{outer}} - A_{\text{inner}}$<br>$183.8235294 = A_{\text{outer}} - (\pi \times 37^2 / 4)$<br>$183.8235294 = A_{\text{outer}} - 1075.210086$<br>$A_{\text{outer}} = 183.8235294 + 1075.210086$<br>$A_{\text{outer}} = 1259.033615 \text{ mm}^2$<br><br>$A = \pi \times d^2 / 4$<br>$d = \sqrt{(1259.033615 \times 4 / \pi)}$<br>$d = 40.03812417 \text{ mm}$<br><br>$\text{thickness} = (40.03812417 - 37) / 2$<br>$\text{thickness} = 1.519062084 \text{ mm}$<br><b>thickness = 1.5mm (2 sf)</b> | 5        | <p>1 mark for effective area.</p> <p>1 mark for <math>A_{\text{inner}}</math>.</p> <p>1 mark for outer area.</p> <p>1 mark for outer diameter.</p> <p>1 mark for thickness, unit required.</p> |
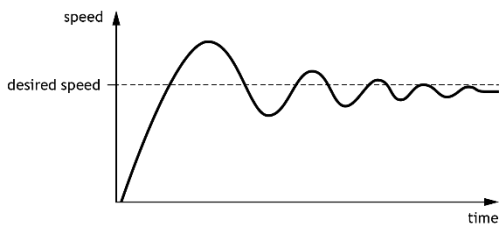
| Question |     |      | Expected response                                                                                                                                                                                                                                            | Max mark | Additional guidance                                                                                                                                |
|----------|-----|------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|----------------------------------------------------------------------------------------------------------------------------------------------------|
| 10.      | (a) | (i)  | Thermistor resistance = 2.0 kΩ<br><br>$I_{\text{therm}} = (5 - 0.70) / 2000$<br>$= 0.00215 \text{ A}$<br>$= 0.0022 \text{ A (2 sf)}$<br>$= 2.2 \text{ mA (2 sf)}$                                                                                            | 3        | 1 mark for correct reading of resistance from graph.<br><br>1 mark for voltage over thermistor.<br><br>1 mark for calculating $I_{\text{therm}}$ . |
|          |     | (ii) | $I_r = 0.70 / 680$<br>$= 0.001029412 \text{ A}$<br><br>$I_b = I_{\text{therm}} - I_r$<br>$= 0.0022 - 0.001029412$<br>$= 0.001170588$<br>$= 1.2 \text{ mA (2 sf)}$                                                                                            | 2        | 1 mark for calculating $I_r$ .<br><br>1 mark for calculating $I_b$ .<br>(FTE applies - 1.1 mA if 2.15 mA given from 10(a)(i)).                     |
|          | (b) |      | The power/motor would either be on or off <b>meaning</b> there would not be a smooth motion.<br><br><b>OR</b><br><br>The power/motor would either be on or off <b>meaning</b> there would be a significant overshoot that would cause over tightening.       | 2        | 1 mark for cause (motor on or off / too fast or too slow).<br><br>1 mark for effect (smooth motion / overshoot / not steady speed).                |
|          | (c) |      | $8.0 = (48 / 12) \times (3.2 - V_{\text{feedback}})$<br><br>$V_{\text{feedback}} = 1.2 \text{ V (2 sf)}$                                                                                                                                                     | 2        | 1 mark for substitution.<br><br>1 mark for feedback voltage.                                                                                       |
|          | (d) |      | <ul style="list-style-type: none"> <li>Initial response would be quicker/steeper.</li> <li>The error reduces over time.</li> <li>Eventually, it would settle.</li> </ul>  | 3        | 1 for each correct comment or illustration.<br><br>3 marks awarded for correctly drawn graph to illustrate each bullet point.                      |

| Question |     |  | Expected response                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                         | Max mark | Additional guidance                                                                                                                                                                                                                                                                                                           |
|----------|-----|--|-----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|
| 10.      | (e) |  | $\Sigma F_v = 0$<br>$753\sin 64 + 877\sin 59 = F_v + 940\sin 47$<br>$676.7919169 + 751.7357227 = F_v + 687.4724795$<br><br>$F_v = 741.0551601 \text{ N}$<br><br>$\Sigma F_H = 0$<br>$877\cos 59 + 940\cos 47 = F_H + 753\cos 64$<br>$451.6883917 + 641.0784585 = F_H + 330.0934735$<br><br>$F_H = 762.6733766 \text{ N}$<br><br>$F = \sqrt{(741.0551601^2 + 762.6733766^2)}$<br>$F = 1063.406521 \text{ N}$<br><b><math>F = 1100 \text{ N (2 sf)}</math></b><br><br>$\theta = \tan^{-1}(741.0551601/762.6733766)$<br>$\theta = 44.17634918^\circ$<br><b><math>\theta = 44^\circ (2 \text{ sf})</math></b> | 6        | <p>1 mark for substitution.</p><br><br><p>1 mark for calculating <math>F_v</math>.</p><br><br><p>1 mark for substitution.</p><br><p>1 mark for calculating <math>F_H</math>.</p><br><br><p>1 mark for calculating <math>F</math>, unit required.</p><br><br><p>1 mark for calculating <math>\theta</math>, unit required.</p> |

| Question |     |  | Expected response                        |       |      |       | Max mark | Additional guidance                                                                                      |
|----------|-----|--|------------------------------------------|-------|------|-------|----------|----------------------------------------------------------------------------------------------------------|
| 11.      | (a) |  | Member                                   | AB    | AE   | BE    | BC       |                                                                                                          |
|          |     |  | Force                                    | 54kN  | 27kN | 2.3kN | 28kN     |                                                                                                          |
|          |     |  | Nature                                   | strut | tie  | tie   | strut    |                                                                                                          |
|          |     |  |                                          |       |      |       |          |                                                                                                          |
|          |     |  |                                          |       |      |       | 6        |                                                                                                          |
|          |     |  | Node A                                   |       |      |       |          |                                                                                                          |
|          |     |  | sin60 = 47/AB                            |       |      |       |          |                                                                                                          |
|          |     |  | AB = 54.27092530 kN                      |       |      |       |          |                                                                                                          |
|          |     |  | AB = 54kN (2 sf)                         |       |      |       |          | 1 mark for calculating AB.                                                                               |
|          |     |  | cos60 = AE/54                            |       |      |       |          |                                                                                                          |
|          |     |  | AE = 27 kN (2 sf)                        |       |      |       |          | 1 mark for calculating AE.                                                                               |
|          |     |  | Node B                                   |       |      |       |          |                                                                                                          |
|          |     |  | ΣF <sub>v</sub> = 0                      |       |      |       |          |                                                                                                          |
|          |     |  | F <sub>vAB</sub> = 45 + F <sub>vBE</sub> |       |      |       |          |                                                                                                          |
|          |     |  | 47 = 45 + BEsin60                        |       |      |       |          |                                                                                                          |
|          |     |  | BE = 2.309401077 kN                      |       |      |       |          |                                                                                                          |
|          |     |  | BE = 2.3 kN (2 sf) (tie)                 |       |      |       |          | 1 mark for calculating BE<br>(accept use of F <sub>vAB</sub> = 54sin60).<br>1 mark for the nature of BE. |
|          |     |  | ΣF <sub>H</sub> = 0                      |       |      |       |          |                                                                                                          |
|          |     |  | BC = F <sub>HAB</sub> + F <sub>HBE</sub> |       |      |       |          |                                                                                                          |
|          |     |  | BC = 54cos60 + 2.3cos60                  |       |      |       |          |                                                                                                          |
|          |     |  | BC = 28.15 kN                            |       |      |       |          |                                                                                                          |
|          |     |  | BC = 28kN (2 sf) (strut)                 |       |      |       |          | 1 mark for calculating BC.<br>1 mark for the nature of BC.                                               |
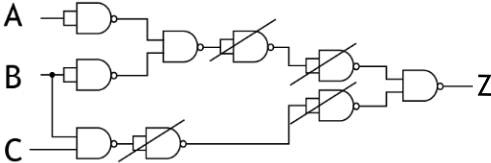
| Question |     |       | Expected response                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | Max mark | Additional guidance                                                                                                                                              |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
|----------|-----|-------|--------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|------------------------------------------------------------------------------------------------------------------------------------------------------------------|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|---|------------------------------------------------------------------------------------------------------------------------------|
| 11.      | (b) | (i)   | <table><tr><th>A</th><th>B</th><th>C</th><th>D</th><th>E</th><th>F</th><th>Z</th></tr><tr><td>0</td><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr><tr><td>0</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td><td>1</td><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>0</td><td>1</td><td>1</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td><td>1</td><td>0</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td><td>0</td><td>0</td><td>1</td><td>0</td></tr></table> | A        | B                                                                                                                                                                | C | D | E | F | Z | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 | 0 | 1 | 0 | 4 | 1 mark for column D.<br>1 mark for column E.<br>1 mark for column F (FTE available).<br>1 mark for column Z (FTE available). |
| A        | B   | C     | D                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | E        | F                                                                                                                                                                | Z |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
| 0        | 0   | 0     | 1                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | 1        | 1                                                                                                                                                                | 1 |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
| 0        | 0   | 1     | 1                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | 0        | 0                                                                                                                                                                | 0 |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
| 0        | 1   | 0     | 1                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | 1        | 0                                                                                                                                                                | 0 |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
| 0        | 1   | 1     | 1                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | 0        | 1                                                                                                                                                                | 1 |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
| 1        | 0   | 0     | 1                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | 1        | 1                                                                                                                                                                | 1 |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
| 1        | 0   | 1     | 1                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | 0        | 0                                                                                                                                                                | 0 |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
| 1        | 1   | 0     | 0                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | 1        | 0                                                                                                                                                                | 0 |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
| 1        | 1   | 1     | 0                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                      | 0        | 1                                                                                                                                                                | 0 |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
|          |     | (ii)  | $Z = \overline{(A+B)} + (B \cdot C)$                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                   | 3        | 1 mark for NOT A+B (with brackets).<br>1 mark for OR.<br>1 mark for B·C.                                                                                         |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
|          |     | (iii) |                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                                       | 4        | 1 mark for NOR NAND with connections.<br><br>1 mark for AND NAND with connections.<br><br>1 mark for OR NAND with connections.<br><br>1 mark for simplification. |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |
|          | (c) |       | Use knowledge of logic gates and their operation to design circuits.<br><br>Use knowledge of Boolean algebra to simplify logic circuit design.<br><br>Use knowledge of truth tables to test logic circuit designs.<br><br>Use knowledge of NAND conversion to simplify circuit construction.<br><br>Use knowledge of digital sensing control circuits to design voltage divider circuits.<br><br>Use knowledge of op amp configurations and their operations to design circuits.<br><br>Use knowledge of control systems using microcontrollers.<br><br>Use knowledge of programming language.<br><br>Use knowledge of interfacing with output circuits.                                                                                               | 2        | Responses must be descriptive.<br><br>1 mark for each valid response.                                                                                            |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |   |                                                                                                                              |



| Question |     |  | Expected response                                                                                                                                                                                                                                                                                                                                                                                                          | Max mark | Additional guidance                                                          |
|----------|-----|--|----------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------|------------------------------------------------------------------------------|
| 11.      | (d) |  | <p>Improved physical health through promotion of walking/running/cycling as mode of transport.</p> <p>Improved social relationships as improved infrastructure means it is easier to meet up with and visit friends/family.</p> <p>Improved mental health as opportunities to go out and socialise are increased.</p> <p>Improved physical health as less pollution in the city.</p> <p>Any other reasonable response.</p> | 2        | <p>Responses must be descriptive.</p> <p>1 mark for each valid response.</p> |

[END OF MARKING INSTRUCTIONS]